

Homework 2: Circuit Emulation (Four Ways)

CIRCUIT DESCRIPTION

Emulate a circuit that takes in 4 inputs (A, B, C, D) and whose output Q is True only when **exactly** 1 of the 4 inputs is **False**.

Introduction

I started with the truth table and easily derived a Boolean expression from it. After the boolean expression, I worked on the circuit diagram, then the Python function. Finishing the assignment off with the optional extra credit simplification. The truth table was the easiest for me. I now have a solid understanding of how to make them. The most challenging was the circuit diagram. I got lost about halfway through and start crossing wires or putting them in the incorrect gate. I find myself starting over multiple times. This time, I labeled the gates as I went, which helped, but I still found I needed more space than I had initially thought for my gates and wires. I regret not spreading out my inputs and gates, which made it hard to keep everything neat as I neared the end.

Truth Table/Test Table

A	B	C	D	Q (expected)	Rc (actual)	Rp (actual)	Subexpression
0	0	0	0	0	0	0	
0	0	0	1	0	0	0	
0	0	1	0	0	0	0	
0	0	1	1	0	0	0	
0	1	0	0	0	0	0	
0	1	0	1	0	0	0	
0	1	1	0	0	0	0	
0	1	1	1	1	1	1	$\sim A \wedge B \wedge C \wedge D$
1	0	0	0	0	0	0	
1	0	0	1	0	0	0	
1	0	1	0	0	0	0	
1	0	1	1	1	1	1	$A \wedge \sim B \wedge C \wedge D$
1	1	0	0	0	0	0	

1	1	0	1	1	1	1	$A \wedge B \wedge \sim C \wedge D$
1	1	1	0	1	1	1	$A \wedge B \wedge C \wedge \sim D$
1	1	1	1	0	0	0	

Boolean Algebra Expression

$$(\sim A \wedge B \wedge C \wedge D) \vee (A \wedge \sim B \wedge C \wedge D) \vee (A \wedge B \wedge \sim C \wedge D) \vee (A \wedge B \wedge C \wedge \sim D)$$

[Optional for extra credit] Simplification

Step 1. Start with $(\sim A \wedge B \wedge C \wedge D) \vee (A \wedge \sim B \wedge C \wedge D) \vee (A \wedge B \wedge \sim C \wedge D) \vee (A \wedge B \wedge C \wedge \sim D)$

Step 2. Group terms using the associative law

$$((\sim A \wedge B \wedge C \wedge D) \vee (A \wedge \sim B \wedge C \wedge D)) \vee ((A \wedge B \wedge \sim C \wedge D) \vee (A \wedge B \wedge C \wedge \sim D))$$

Step 3 Factor the like terms in the first group using the distributive law

$$(C \wedge D \wedge ((\sim A \wedge B) \vee (A \wedge \sim B)))$$

Step 4 Factor the like terms second group using the distributive law

$$(A \wedge B \wedge ((\sim C \wedge D) \vee (C \wedge \sim D)))$$

Step 5 Combine the expressions

$$(C \wedge D \wedge ((\sim A \wedge B) \vee (A \wedge \sim B))) \vee (A \wedge B \wedge ((\sim C \wedge D) \vee (C \wedge \sim D)))$$

Tyler Velez

return gate19

print(circuit(0, 1, 1, 1))